

**Problem 1** (3 points)

Two conducting wires in the shape of cylinders of the same cross-sectional area, at  $0^\circ\text{C}$  have resistivities  $\rho_{01}$ ,  $\rho_{02}$  and temperature coefficients of resistivity  $\alpha_1$  and  $\alpha_2$ , respectively. What is the effective temperature coefficient of resistivity if the conductors are connected (a) in series, (b) in parallel.

**Solution:**

We may as well assume both the two conducting wires have the same length. Then we denote their resistance

$$R_1 = \rho_1 \frac{L}{A}$$

$$R_2 = \rho_2 \frac{L}{A}$$

Then for **series**, the cross-sectional area will not change but the length doubles.

$$R_s = \rho_s \frac{2L}{A} = R_1 + R_2$$

Hence

$$\rho_s = \frac{\rho_1 + \rho_2}{2} \quad (1)$$

For **parallel**, the length will not change but the cross-sectional area doubles.

$$R_p = \rho_p \frac{L}{2A} = \frac{R_1 R_2}{R_1 + R_2}$$

Hence

$$\rho_p = \frac{2\rho_1\rho_2}{\rho_1 + \rho_2} \quad (2)$$

While we know

$$\rho_i = \rho_{0i}(1 + \alpha_i(T - T_0)) \quad \text{where } i = 1, 2 \quad (3)$$

Namely

$$\begin{aligned} \rho_{0s}(1 + \alpha_s(T - T_0)) &= \frac{\rho_{01} + \rho_{02}}{2}(1 + \alpha_s(T - T_0)) = \frac{\rho_{01}(1 + \alpha_1(T - T_0)) + \rho_{02}(1 + \alpha_2(T - T_0))}{2} \\ \frac{2\rho_{01}\rho_{02}}{\rho_{01} + \rho_{02}}(1 + \alpha_p(T - T_0)) &= \frac{2\rho_{01}(1 + \alpha_1(T - T_0))\rho_{02}(1 + \alpha_2(T - T_0))}{\rho_{01}(1 + \alpha_1(T - T_0)) + \rho_{02}(1 + \alpha_2(T - T_0))} \end{aligned}$$


while  $T_0 = 0$ , hence

$$\alpha_s = \frac{\rho_{01}\alpha_1 + \rho_{02}\alpha_2}{\rho_{01} + \rho_{02}} \quad (4)$$

$$\alpha_p = \frac{\rho_{01}\alpha_2 + \rho_{02}\alpha_1 + (\rho_{01} + \rho_{02})\alpha_1\alpha_2(T - T_0)}{\rho_{01} + \rho_{02} + \rho_{01}\alpha_1(T - T_0) + \rho_{02}\alpha_2(T - T_0)} = \frac{\rho_{01}\alpha_2 + \rho_{02}\alpha_1 + (\rho_{01} + \rho_{02})\alpha_1\alpha_2T}{\rho_{01} + \rho_{02} + \rho_{01}\alpha_1T + \rho_{02}\alpha_2T} \quad (5)$$

**Problem 2** (4 points)

For the system of resistors shown in the figure, find the equivalent resistance between points A and B.

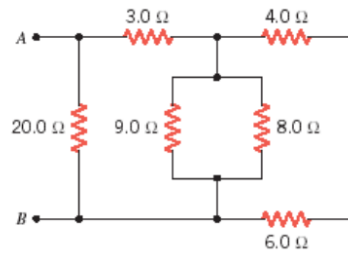**Solution:**

We first analyze the circuit diagram as follows.

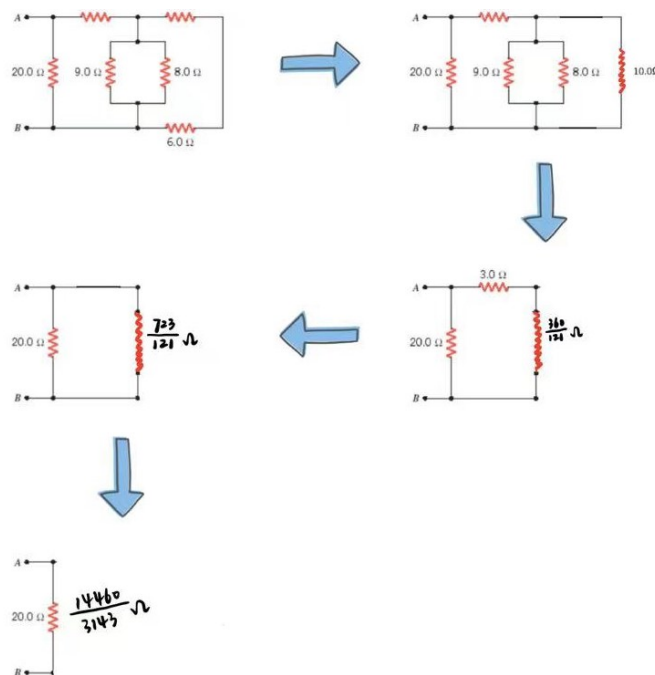


Figure 1: Analysis Process

As the diagram shows, we calculate the parallel resistance with  $4\Omega$  and  $6\Omega$  being a series first.

$$R_p = \frac{1}{\frac{1}{9} + \frac{1}{8} + \frac{1}{4+6}} = \frac{360}{121} [\Omega]$$

Then calculate the series

$$R_s = 3 + \frac{360}{121} = \frac{723}{121} [\Omega]$$


At last calculate the **equivalent resistance**

$$R_{eq} = \frac{1}{\frac{1}{20} + \frac{1}{723/121}} = \frac{14460}{3143} [\Omega] \quad (6)$$

**Problem 3** (4 points)

Twelve identical resistors, each of resistance  $R$ , are connected to form a cube-shaped circuit (see the figure). Find the equivalent resistance between points  $A$  and  $B$ .

*Hint: Use symmetry.*

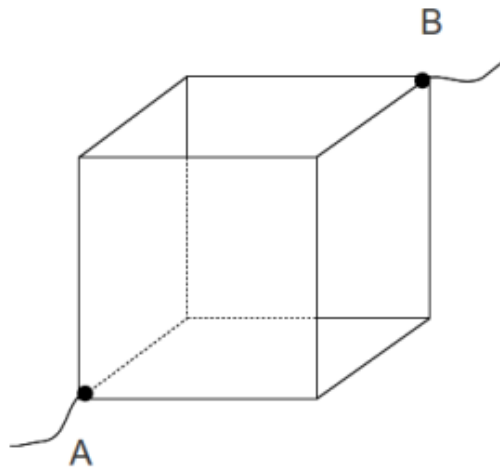**Solution:**

We may first consider the symmetry to divide the cube into three parts as follows.

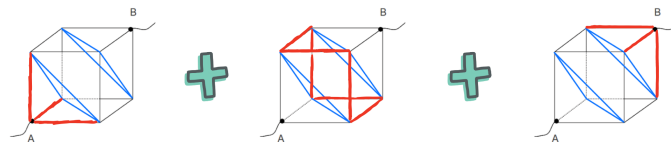


Figure 2: Symmetry Analysis

Apparently, it is equivalent to three resistors in series which are all composed of parallel resistors, shown as follows.

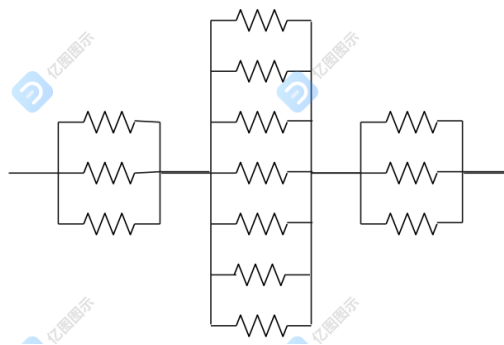


Figure 3: Equivalent Circuit

We then calculate the equivalent resistance separately.

For the left side

$$R_{left} = \frac{R}{3}$$

For the middle part

$$R_{middle} = \frac{R}{6}$$

For the right side

$$R_{right} = \frac{R}{3}$$


Hence the total equivalent resistance is

$$R_{eq} = \frac{5R}{6} \quad (7)$$

**Problem 4** (5 points)

Consider the circuit shown in the figure below ( $E_1 = 12 \text{ V}$ ,  $E_2 = 8 \text{ V}$ ,  $r = 1 \Omega$ ,  $R = 8 \Omega$ ).

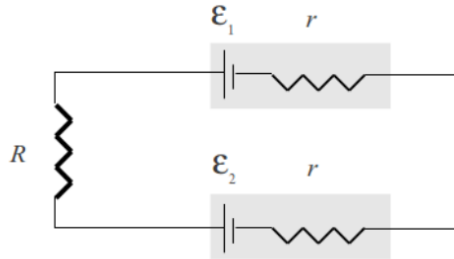- (a) Find the current through the resistor  $R$ ,
- (b) and the total rate of dissipation of electrical energy in the resistor  $R$  and in the internal resistance of the batteries.
- (c) In one of the batteries, chemical energy is being converted into electrical energy. In which one it is happening, and at what rate?
- (d) In one of the batteries, electrical energy is being converted into chemical energy. In which one it is happening, and at what rate?
- (e) Show that the overall rate of production of electrical energy is equal to the overall rate of consumption of electrical energy in the circuit.



**Solution:**

- (a) Suppose there is a current flowing clockwise, whose magnitude is  $i$ . Then

$$\varepsilon_1 + 2ir + iR - \varepsilon_2 = 0 \quad (8)$$

$$\Rightarrow i = -0.4 \text{ [A]} \quad (9)$$

Showing that the current is flowing counter-clockwise with magnitude of  $0.4 \text{ A}$ .

- (b) The rate of dissipation of electrical energy is equal to the power of elements. Hence

$$P_R = i^2 R = 1.28 \text{ [W]}$$

$$P_r = 2i^2 r = 0.32 \text{ [W]}$$

(c)  $\varepsilon_1$ ,  $P_1 = 12 \times 0.4 = 4.8 \text{ [J/s]}$ .

(d)  $\varepsilon_2$ ,  $P_2 = 8 \times 0.4 = 3.2 \text{ [J/s]}$ .


(e) Notice that

$$P_R + P_r + P_2 = P_1 \quad (10)$$

Namely, the rates of consumption and production are identical.

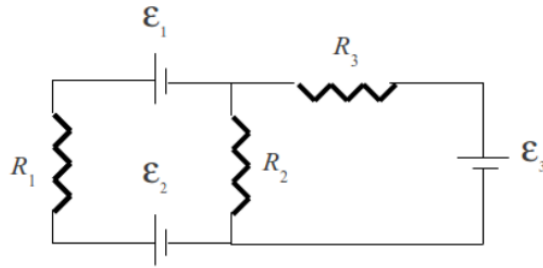**Problem 5** (4 points)

For the circuit shown in the figure below, find the current through each of the resistors. For numerical calculations assume:  $R_1 = 2\Omega$ ,  $R_2 = 4\Omega$ ,  $R_3 = 5\Omega$ ,  $\varepsilon_1 = 20V$ ,  $\varepsilon_2 = 14V$ ,  $\varepsilon_3 = 36V$ . The internal resistance of the emfs is negligible.



**Solution:**

Suppose the current in the left loop(mesh) is  $i_1$ , and the current in the right loop(mesh) is  $i_2$ . Then we have

$$-\varepsilon_1 + i_1 R_1 + \varepsilon_2 + (i_1 - i_2) R_2 = 0 \quad (11)$$

$$-\varepsilon_3 + i_2 R_3 + (i_2 - i_1) R_2 = 0 \quad (12)$$

Then we get

$$\begin{cases} i_1 = \frac{99}{19} [A] \\ i_2 = \frac{120}{19} [A] \end{cases} \quad (13)$$

Hence we know the current passing through each resistor.

$$i_{R_1} = \frac{99}{19} [A] \quad i_{R_2} = \frac{21}{19} [A] \quad i_{R_3} = \frac{120}{99} [A] \quad (14)$$


**Problem 6** (3 points)

For the circuit shown in the figure below what happens to the brightness of the bulbs when the switch  $S$  is closed if the battery (a) has no internal resistance and (b) has non-negligible internal resistance? Explain why.

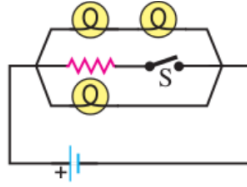
**Solution:**

For (a), the brightness of the bulb will not change since the voltage applied on the bulb has not changed. The **terminal voltage** is still equal to **emf**.

For (b), the brightness of the bulb will decrease since the whole resistance of the system will decrease when the switch closed, thus the **terminal voltage** will decrease as well. Hence the brightness decreases.



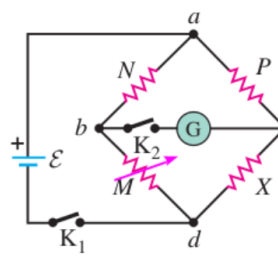**Problem 7** (4 points) Four resistors are connected to form a Wheatstone bridge - a circuit that can be used to measure unknown resistance  $X$ , provided the resistances of  $N$ ,  $M$  and  $P$  are known. The idea of the measurement method is to tune (with the switches  $K_1$  and  $K_2$  closed) the variable resistance  $M$  so that the potential difference between points  $b$  and  $c$  is zero and the galvanometer does not show any current. The bridge is then said to be balanced. Show that in this configuration  $X = MP/N$ .



**Solution:** Suppose the current flowing in  $a-b-d$  is  $i_1$  while the current flowing in  $a-c-d$  is  $i_2$ . Then according to KVL

$$i_1(N + M) - i_2(P + X) = 0 \quad (15)$$

$$(16)$$

According to the balance condition

$$\varepsilon - i_1 N = \varepsilon - i_2 P \quad (17)$$

Hence

$$\frac{N}{P} = \frac{i_2}{i_1} = \frac{N + M}{P + X}$$

Hence

$$\frac{N}{P} = \frac{M}{X}$$

Namely

$$X = \frac{MP}{N} \quad (18)$$

**Problem 8** (3 points) Strictly speaking, the formula  $q(t) = Q_{\max} e^{-t/RC}$  implies that an infinite amount of time is required to discharge a capacitor in a  $R-C$  circuit completely. Yet for practical purposes, a capacitor may be considered to be fully discharged after a finite time  $t_d$ , defined as the time when the charge on the capacitor  $q(t_d)$  differs from zero by no more than the charge of one electron.

(a) Find  $t_d$  if  $C = 0.92 \mu\text{F}$ ,  $R = 670 \text{k}\Omega$ , and  $Q_{\max} = 7 \mu\text{C}$ .

- (b) For a given  $Q_{\max}$  is the time required to reach this state always the same number of time constants, independent of  $R$  and  $C$ . Why or why not?

**Solution:**

- (a) Plug in the data

$$\begin{aligned} q_e &= Q_{\max}^{-\frac{t_d}{RC}} \\ \Rightarrow t_d &= 19.36 \text{ [s]} \end{aligned}$$

- (b) Based on (a)

$$\ln\left(\frac{q_e}{Q_{\max}}\right) = -\frac{t_d}{RC} \tag{19}$$

Hence we conclude that,  $t_d$  does not depend on  $R$  or  $C$  separately but depend on  $RC$  as a whole. Namely, if  $RC$  is constant,  $t_d$  is also a constant.