

Problem 1 (3 points)

Two conducting wires in the shape of cylinders of the same cross-sectional area, at 0°C have resistivities ρ_{01} , ρ_{02} and temperature coefficients of resistivity α_1 and α_2 , respectively. What is the effective temperature coefficient of resistivity if the conductors are connected (a) in series, (b) in parallel.

Solution:

We may as well assume both the two conducting wires have the same length. Then we denote their resistance

$$R_1 = \rho_1 \frac{L}{A}$$
$$R_2 = \rho_2 \frac{L}{A}$$

Then for **series**, the cross-sectional area will not change but the length doubles.

$$R_s = \rho_s \frac{2L}{A} = R_1 + R_2$$

Hence

$$\rho_s = \frac{\rho_1 + \rho_2}{2} \tag{1}$$

For **parallel**, the length will not change but the cross-sectional area doubles.

$$R_p = \rho_p \frac{L}{2A} = \frac{R_1 R_2}{R_1 + R_2}$$

Hence

$$\rho_p = \frac{2\rho_1\rho_2}{\rho_1 + \rho_2} \tag{2}$$

While we know

$$\rho_i = \rho_{0i}(1 + \alpha_i(T - T_0)) \quad \text{where } i = 1, 2 \tag{3}$$

Namely

$$\rho_{0s}(1 + \alpha_s(T - T_0)) = \frac{\rho_{01} + \rho_{02}}{2}(1 + \alpha_s(T - T_0)) = \frac{\rho_{01}(1 + \alpha_1(T - T_0)) + \rho_{02}(1 + \alpha_2(T - T_0))}{2}$$
$$\frac{2\rho_{01}\rho_{02}}{\rho_{01} + \rho_{02}}(1 + \alpha_p(T - T_0)) = \frac{2\rho_{01}(1 + \alpha_1(T - T_0))\rho_{02}(1 + \alpha_2(T - T_0))}{\rho_{01}(1 + \alpha_1(T - T_0)) + \rho_{02}(1 + \alpha_2(T - T_0))}$$


Hence

$$\alpha_s = \frac{\rho_{01}\alpha_1 + \rho_{02}\alpha_2}{\rho_{01} + \rho_{02}} \tag{4}$$

$$\alpha_p = \frac{\rho_{01}\alpha_2 + \rho_{02}\alpha_1 + (\rho_{01} + \rho_{02}\alpha_1\alpha_2(T - T_0))}{\rho_{01} + \rho_{02} + \rho_{01}\alpha_1(T - T_0) + \rho_{02}\alpha_2(T - T_0)} \tag{5}$$

Problem 2 (4 points)

For the system of resistors shown in the figure, find the equivalent resistance between points A and B.

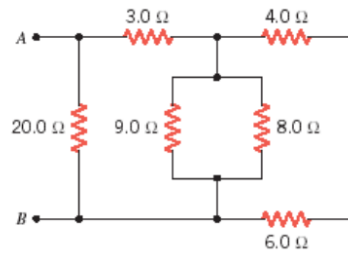**Solution:**

We first analyze the circuit diagram as follows.

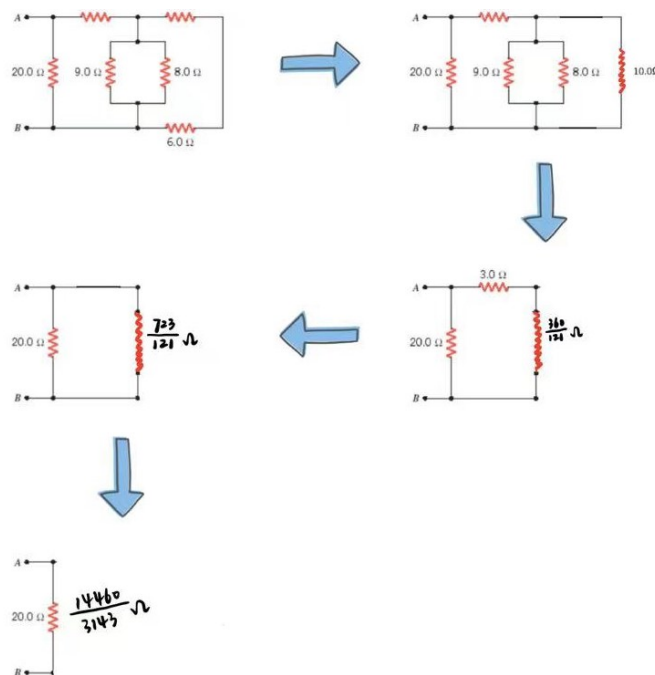


Figure 1: Analysis Process

As the diagram shows, we calculate the parallel resistance with 4Ω and 6Ω being a series first.

$$R_p = \frac{1}{\frac{1}{9} + \frac{1}{8} + \frac{1}{4+6}} = \frac{360}{121} [\Omega]$$

Then calculate the series

$$R_s = 3 + \frac{360}{121} = \frac{723}{121} [\Omega]$$


At last calculate the **equivalent resistance**

$$R_{eq} = \frac{1}{\frac{1}{20} + \frac{1}{723/121}} = \frac{14460}{3143} [\Omega] \quad (6)$$

Problem 3 (4 points)

Twelve identical resistors, each of resistance R , are connected to form a cube-shaped circuit (see the figure). Find the equivalent resistance between points A and B .

Hint: Use symmetry.

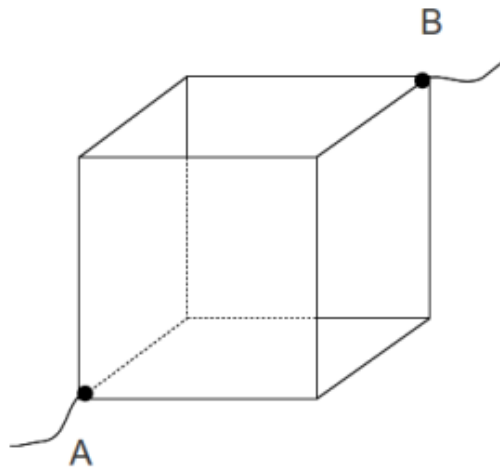**Solution:**

We may first consider the symmetry to divide the cube into three parts as follows.

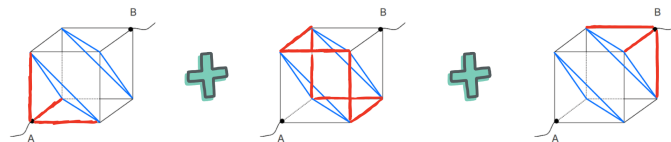


Figure 2: Symmetry Analysis

Apparently, it is equivalent to three resistors in series which are all composed of parallel resistors, shown as follows.

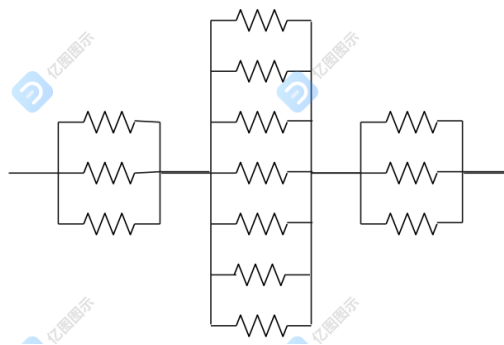


Figure 3: Equivalent Circuit

We then calculate the equivalent resistance separately.

For the left side

$$R_{left} = \frac{R}{3}$$

For the middle part

$$R_{middle} = \frac{R}{6}$$

For the right side

$$R_{right} = \frac{R}{3}$$


Hence the total equivalent resistance is

$$R_{eq} = \frac{5R}{6} \quad (7)$$

Problem 4 (5 points)

Consider the circuit shown in the figure below ($E_1 = 12 \text{ V}$, $E_2 = 8 \text{ V}$, $r = 1 \Omega$, $R = 8 \Omega$).

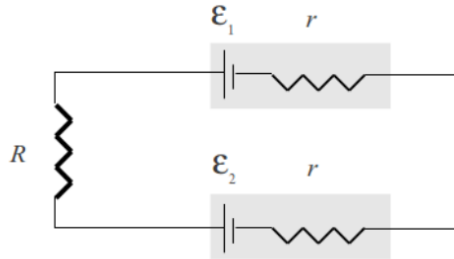- (a) Find the current through the resistor R ,
- (b) and the total rate of dissipation of electrical energy in the resistor R and in the internal resistance of the batteries.
- (c) In one of the batteries, chemical energy is being converted into electrical energy. In which one it is happening, and at what rate?
- (d) In one of the batteries, electrical energy is being converted into chemical energy. In which one it is happening, and at what rate?
- (e) Show that the overall rate of production of electrical energy is equal to the overall rate of consumption of electrical energy in the circuit.



Solution:

- (a) Suppose there is a current flowing clockwise, whose magnitude is i . Then

$$\varepsilon_1 + 2ir + iR - \varepsilon_2 = 0 \quad (8)$$

$$\Rightarrow i = -0.4 \text{ [A]} \quad (9)$$

Showing that the current is flowing counter-clockwise with magnitude of 0.4 A .

- (b) The rate of dissipation of electrical energy is equal to the power of elements. Hence

$$P_R = i^2 R = 1.28 \text{ [W]}$$

$$P_r = 2i^2 r = 0.32 \text{ [W]}$$

(c) ε_1 , $P_1 = 12 \times 0.4 = 4.8 \text{ [J/s]}$.

(d) ε_2 , $P_2 = 8 \times 0.4 = 3.2 \text{ [J/s]}$.


(e) Notice that

$$P_R + P_r + P_2 = P_1 \quad (10)$$

Namely, the rates of consumption and production are identical.

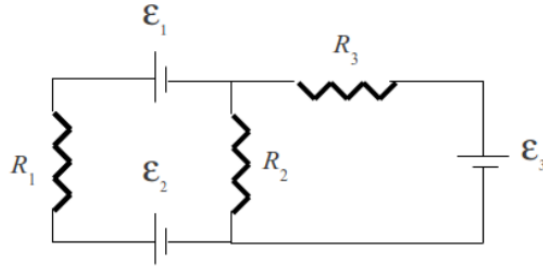Problem 5 (4 points)

For the circuit shown in the figure below, find the current through each of the resistors. For numerical calculations assume: $R_1 = 2\Omega$, $R_2 = 4\Omega$, $R_3 = 5\Omega$, $\varepsilon_1 = 20V$, $\varepsilon_2 = 14V$, $\varepsilon_3 = 36V$. The internal resistance of the emfs is negligible.



Solution:

Suppose the current in the left loop(mesh) is i_1 , and the current in the right loop(mesh) is i_2 . Then we have

$$-\varepsilon_1 + i_1 R_1 + \varepsilon_2 + (i_1 - i_2) R_2 = 0 \quad (11)$$


$$\varepsilon_3 + i_2 R_3 + (i_2 - i_1) R_2 = 0 \quad (12)$$

Then we get

$$\begin{cases} i_1 = -\frac{45}{19} [A] \\ i_2 = -\frac{96}{19} [A] \end{cases} \quad (13)$$

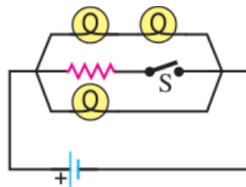Problem 6 (3 points)

For the circuit shown in the figure below what happens to the brightness of the bulbs when the switch S is closed if the battery (a) has no internal resistance and (b) has non-negligible internal resistance? Explain why.




Solution:

For (a), the brightness of the bulb will not change since the voltage applied on the bulb has not changed. The **terminal voltage** is still equal to **emf**.

For (b), the brightness of the bulb will decrease since the whole resistance of the system will decrease when the switch closed, thus the **terminal voltage** will decrease as well. Hence the brightness decreases.

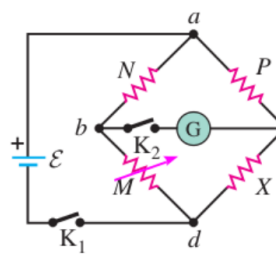Problem 7 (*4 points*) Four resistors are connected to form a Wheatstone bridge - a circuit that can be used to measure unknown resistance X , provided the resistances of N , M and P are known. The idea of the measurement method is to tune (with the switches K_1 and K_2 closed) the variable resistance M so that the potential difference between points b and c is zero and the galvanometer does not show any current. The bridge is then said to be balanced. Show that in this configuration $X = MP/N$.



Solution: Suppose the current flowing in a-b-d is i_1 while the current flowing in a-c-d is i_2 . Then according to KVL

$$i_1(N + M) - i_2(P + X) = 0 \quad (14)$$

$$(15)$$

According to the balance condition

$$\varepsilon - i_1 N = \varepsilon - i_2 P \quad (16)$$

Hence

$$\frac{N}{P} = \frac{i_2}{i_1} = \frac{N + M}{P + X}$$

Hence

$$\frac{N}{P} = \frac{M}{X}$$

Namely

$$X = \frac{MP}{N} \quad (17)$$

Problem 8 (*3 points*) Strictly speaking, the formula $q(t) = Q_{\max} e^{-t/RC}$ implies that an infinite amount of time is required to discharge a capacitor in a $R-C$ circuit completely. Yet for practical purposes, a capacitor may be considered to be fully discharged after a finite time t_d , defined as the time when the charge on the capacitor $q(t_d)$ differs from zero by no more than the charge of one electron.

- Find t_d if $C = 0.92\mu\text{F}$, $R = 670\text{k}\Omega$, and $Q_{\max} = 7\mu\text{C}$.
- For a given Q_{\max} is the time required to reach this state always the same number of time constants, independent of R and C . Why or why not?

Solution:

(a) Plug in the data

$$\begin{aligned} q_e &= Q_{max}^{-\frac{t_d}{RC}} \\ \Rightarrow t_d &= 19.36 \text{ [s]} \end{aligned}$$

(b) Based on (a)

$$\ln \left(\frac{q_e}{Q_{max}} \right) = -\frac{t_d}{RC} \tag{18}$$

Hence we conclude that, t_d does not depend on R or C separately but depend on RC as a whole.